



1. State table

Current state	Inputs (loop, reset)	Next State
State 1	Loop = 1, reset = 0	State 6
State 1	Loop = 0, reset = 0	State 2
State 2	Loop = 1, reset = 0	State 7
State 2	Loop = 0, reset = 0	State 3
State 3	Loop = 1, reset = 0	State 7
State 3	Loop = 0, reset = 0	State 6
State 6	Loop = 1, reset = 0	State 2
State 6	Loop = 0, reset = 0	State 7
State 7	Loop = 1, reset = 0	State 1
State 7	Loop = 0, reset = 0	State 6
All States	Reset=1	Reset

2. LED PWM State

State	LED1 (PWM)	LED2 (PWM)	LED3 (PWM)	Encoded (PWM)	S2,S1,S0
State 1	255	0	0	001	S2=0, S1=0, S0=1
State 2	0	255	0	010	S2 = 0, S1 = 1, S0 = 0
State 3	0	0	255	011	S2 = 0, S1 = 1, S0 = 1
State 4	255	255	255	100	S2 = 1, S1 = 0, S0 = 0
State 5	0	0	0	101	S2 = 1, S1 = 0, S0 = 1
State 6	255	255	0	110	S2 = 1, S1 = 1, S0 = 0
State 7	128	0	128	111	S2 = 1, S1 = 1, S0 = 1

S2: most significant bit

S1: Middle bit

S3: Least significant bit

LED 1 PWM Expression:

$$\text{LED1} = S2 * \overline{s1} * S0 + S2 * S1 * \overline{s0} + \overline{s2} * S1 * \overline{s0}$$

LED 2 PWM Expression:

$$\text{LED2} = S2 * S1 * \overline{s0} + \overline{s2} * S1 * S0$$

LED 3 PWM Expression:

$$\text{LED3} = S2 * \overline{s1} * S0 + s2 * S1 * S0$$

3. Encoded 2 bits LED PWM

PWM Value	Encoded
0	00
128	01
255	10

4. Encoded 2 bits LEDs

State	LED1	LED2	LED3
001	10	00	00
010	00	10	00
011	00	00	10
100	10	10	10
101	00	00	00

110	10	10	00
111	01	00	01